

Unit 2

Boolean Algebra


Logic Circuits (Spring 2022)

Introduction


- Two-state variables
 - All switching devices are two-state devices
 - All variables assume only one of two values
 - *Boolean variable* X or Y: input or output of switching circuit
- Symbols “0” and “1”
 - Represent states in a logic circuit (not a numeric value)
 - 0 usually represents range of low voltages and 1 represents range of high voltages in a logic gate circuit
 - 0 represents open switch and 1 represents closed switch in a switching circuit
 - 0 and 1 can represent the two states in any binary valued system
- *Boolean algebra*
 - All variables assume only one of two states
 - Some limited operations are defined on those variables

Basic Operations

 - Basic operations of Boolean (switching) algebra
 - AND
 - OR
 - Complement (or inverse)
- Switch contact



 - Labeled with a variable
- NC(normally closed) and NO(normally open) contacts are always in opposite states



- Variable X is assigned to NO contact $\Rightarrow X'$ will be assigned for NC

Basic Operations: Complement



- Complementation
 - Prime (') denotes complementation
 - $0' = 1$ and $1' = 0$
 - $X' = 1$ if $X = 0$ and $X' = 0$ if $X = 1$
- Complementation is also called inversion
 - Circle at the output denotes inversion



Basic Operations: AND

■ Series switching circuits

A	B	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

  

$C = 0 \rightarrow$ open circuit between terminals 1 and 2
 $C = 1 \rightarrow$ closed circuit between terminals 1 and 2


■ AND operation

- Written algebraically as $C = A \cdot B$
- We will usually write AB instead of $A \cdot B$
- Also referred to as logical (or Boolean) multiplication

Basic Operations: OR

■ Parallel switching circuits

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

 

a closed circuit if either A or B, or both, are closed
 an open circuit only if A and B are both open

■ OR operation

- Written algebraically as $C = A + B$
- Also referred to as logical (or Boolean) addition

Exclusive-OR

- Definition: $X \oplus Y = 1$ iff $X = 1$ or $Y = 1$, but not both


$$0 \oplus 0 = 0 \quad 0 \oplus 1 = 1$$

$$1 \oplus 0 = 1 \quad 1 \oplus 1 = 0$$

- Truth table

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- Logic symbol

 

Exclusive-OR

- Some Theorems

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$

$$X \oplus Y = Y \oplus X \text{ (commutative law)}$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z \text{ (associative law)}$$

$$X(Y \oplus Z) = XY \oplus XZ \text{ (distributive law)}$$

$$(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y'$$

Equivalence Operations

- Definition: $X \equiv Y = 1$ iff X and Y have the same value


$$(0 \equiv 0) = 1 \quad (0 \equiv 1) = 0$$

$$(1 \equiv 0) = 0 \quad (1 \equiv 1) = 1$$

- Truth table

X	Y	$X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- Logic symbol

 

Exclusive OR vs. Equivalence

- Logic expressions

- $X \oplus Y = XY' + X'Y$

- $X \equiv Y = XY + X'Y'$

- Equivalence is the complement of exclusive-OR and vice versa

- $(XY' + X'Y)' = XY + X'Y'$

- $(XY + X'Y')' = XY' + X'Y$

Boolean Expression and Logic Diagram


■ Example Boolean expression

$$AB' + C \quad (2-1)$$

$$[A(C + D)]' + BE \quad (2-2)$$

■ Order of operations: parentheses – inversion – AND – OR

■ Logic diagram

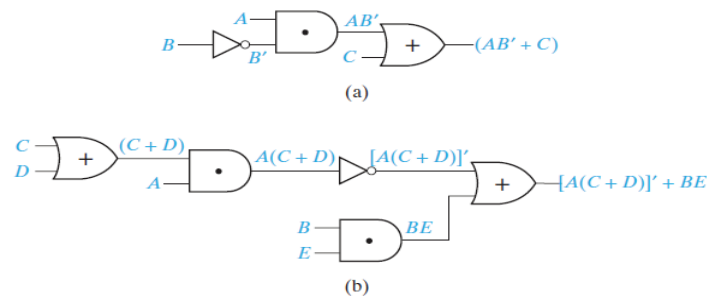

Logic Diagram and Truth Table

■ Logic diagram



■ Truth table

- Specifies the values of a Boolean expression for every possible combination of values of the variables in the expression
- n -variable expression $\Rightarrow 2^n$ rows

A	B	A'	$F = A' + B$
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

Boolean Expressions

- Two Boolean expressions are *equal*
 - If they have the same value for *every* possible combination of the variables

A B C	B'	AB'	AB' + C	A + C	B' + C	(A + C)(B' + C)
0 0 0	1	0	0	0	1	0
0 0 1	1	0	1	1	1	1
0 1 0	0	0	0	0	0	0
0 1 1	0	0	1	1	1	1
1 0 0	1	1	1	1	1	1
1 0 1	1	1	1	1	1	1
1 1 0	0	0	0	1	0	0
1 1 1	0	0	1	1	1	1

$$AB' + C = (A + C)(B' + C) \quad (2-3)$$

Basic Theorems

Operations with 0 and 1:

1. $X + 0 = X$

1D. $X \cdot 1 = X$

2. $X + 1 = 1$

2D. $X \cdot 0 = 0$

Idempotent laws:

3. $X + X = X$

3D. $X \cdot X = X$

Involution law:

4. $(X')' = X$

Laws of complementarity:

5. $X + X' = 1$

5D. $X \cdot X' = 0$

Basic Theorems

Commutative laws:

6. $X + Y = Y + X$

6D. $XY = YX$

Associative laws:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

7D. $(XY)Z = X(YZ) = XYZ$

Distributive laws:

8. $X(Y + Z) = XY + XZ$

8D. $X + YZ = (X + Y)(X + Z)$

DeMorgan's laws:

9. $(X + Y)' = X'Y'$

9D. $(XY)' = X' + Y'$

Basic Theorems

■ Commutative law

- Order in which variables are written does not affect result of applying AND and OR operations
- $XY = YX$
- $X + Y = Y + X$

■ Associative law

- Result of AND and OR operations is independent of which variables we associate together first
- $(XY)Z = X(YZ) = XYZ$
- $(X + Y) + Z = X + (Y + Z) = X + Y + Z$

Basic Theorems

■ Distributive laws

- $X(Y+Z) = XY + XZ$
- $X+YZ = (X+Y)(X+Z) \Leftarrow$ valid for Boolean algebra only

■ DeMorgan's laws

- $(X+Y)' = X'Y'$
- $(XY)' = X' + Y'$

X	Y	X'Y'	X+Y	(X+Y)'	X'Y'	XY	(XY)'	X'+Y'
0	0	1	0	1	1	0	1	1
0	1	1	1	0	0	0	1	1
1	0	0	1	0	0	0	1	1
1	1	0	1	0	0	1	0	0

Simplification Theorems

Uniting theorems:

1. $XY + XY' = X$

1D. $(X + Y)(X + Y') = X$

Absorption theorems:

2. $X + XY = X$

2D. $X(X + Y) = X$

Elimination theorems:

3. $X + X'Y = X + Y$

3D. $X(X' + Y) = XY$

Duality:

4. $(X + Y + Z + \dots)^D = XYZ \dots$

4D. $(XYZ \dots)^D = X + Y + Z + \dots$

Theorems for multiplying out and factoring:

5. $(X + Y)(X' + Z) = XZ + X'Y$

5D. $XY + X'Z = (X + Z)(X' + Y)$

Consensus theorems:

6. $XY + YZ + X'Z = XY + X'Z$

6D. $(X + Y)(Y + Z)(X' + Z) = (X + Y)(X' + Z)$

Simplification Theorems

■ How to prove the simplification theorems

- Using a truth table
- Using the basic theorems

$$XY + XY' = X(Y + Y') = X(1) = X$$

$$X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$$

$$X + X'Y = (X + X')(X + Y) = 1(X + Y) = X + Y$$

$$XY + X'Z + YZ = XY + X'Z + (1)YZ =$$

$$XY + X'Z + (X + X')YZ = XY + XYZ + X'Z + X'YZ =$$

$$XY + X'Z \text{ (using absorption twice)}$$

Consensus Theorem

■ Consensus theorem

- $XY + X'Z + YZ = XY + X'Z$
- $(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

■ Consensus term

- The eliminated term
- YZ
- $Y + Z$

■ Cases of utilizing Consensus theorem

$$a'b' + ac + bc' + b'c + ab = a'b' + ac + bc'$$

$$(a + b + c')(a + b + d')(b + c + d') = (a + b + c')(b + c + d')$$

Simplifying Boolean Expression

Example 2

Simplify $Z = [A + B'C + D + EF] [A + B'C + (D + EF)']$

Substituting: $Z = [X + Y] [X + Y']$

Then, by the uniting theorem (2-15D), the expression reduces to

$$Z = X = A + B'C$$

Simplifying Boolean Expression

Example 3

Simplify $Z = (AB + C) (B'D + C'E') + (AB + C)'$

Substituting: $Z = \underbrace{X'}_{(AB + C)'} + \underbrace{Y}_{(B'D + C'E')}$

By the elimination theorem (2-17): $Z = X + Y = B'D + C'E' + (AB + C)'$

Note that in this example we let $X = (AB + C)'$ rather than $(AB + C)$ in order to match the form of the elimination theorem (2-17).

Complementing Boolean Expression

- Successive application of DeMorgan's laws
 - The complement or inverse of any Boolean expression can be found using DeMorgan's Laws

$$(X_1 + X_2 + X_3 + \cdots + X_n)' = X_1' X_2' X_3' \cdots X_n'$$

$$(X_1 X_2 X_3 \cdots X_n)' = X_1' + X_2' + X_3' + \cdots + X_n'$$

For example, for $n = 3$,

$$(X_1 + X_2 + X_3)' = (X_1 + X_2)' X_3' = X_1' X_2' X_3'$$

- The complement of the product is the sum of the complements
- The complement of the sum is the product of the complements

Complementing Boolean Expression

Example 1

To find the complement of $(A' + B)C'$, first apply (2-13) and then (2-12).

$$[(A' + B)C']' = (A' + B)' + (C')' = AB' + C$$

Complementing Boolean Expression

Example 2

$$\begin{aligned} [(AB' + C)D' + E]' &= [(AB' + C)D']'E' && \text{(by (2-12))} \\ &= [(AB' + C)' + D]E' && \text{(by (2-13))} \\ &= [(AB')'C' + D]E' && \text{(by (2-12))} \\ &= [(A' + B)C' + D]E' && \text{(by (2-13)) (2-27)} \end{aligned}$$

Note that in the final expressions, the complement operation is applied only to single variables.