


# Unit 9

## Multiplexers, Decoders, and Programmable Logic Devices

Logic Circuits (Spring 2022)

 
### Multiplexers

- Multiplexer (MUX)
  - Data selector
  - Takes a group of data input and a group of control inputs
  - Control inputs are used to select one of the data inputs and connect it to the output terminal
- Example: 2-to-1 Multiplexer




# Multiplexers

## 4-to-1 Multiplexer

 

$$Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$


## 2<sup>n</sup>-to-1 Multiplexer

 

$$Z = \sum_{k=0}^{2^n-1} m_k I_k$$

## 8-to-1 Multiplexer


### AND-OR circuit implementation

 


$$Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3 + AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$$

# 8-to-1 Multiplexer

2-level MUX implementation

 


NAND implementation

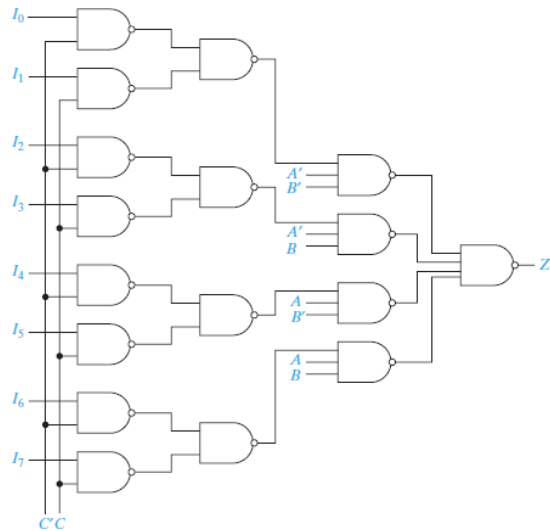

 
## Quad 2-to-1 Multiplexer

- Quad multiplexer
  - Four multiplexer working homogeneously together
  - Selects one of “4-bit data words”
- 2-to-1 multiplexer
  - Selects one of two data



 
## Multiplexers with Enable

- Additional “enable” signal
  - An additional input
  - If  $E = 1$ , the multiplexer functions as an ordinary multiplexer
  - If  $E = 0$ , the multiplexer does not deliver any input to the output
- Active high or active low



## Implementation of a 4-Variable Function (1)


### MUX implementation

 

$$\begin{aligned}
 Z &= C'D'(A' + B') + C'D(A') + CD'(AB' + A'B) + CD(0) \\
 &= A'C' + A'BD' + AB'D'
 \end{aligned}$$
 
# Buffers



- Why buffers?
  - A gate output can only be connected to a limited number of other device inputs without degrading the digital system's performance
  - A simple buffer may be used to increase the driving capability of a gate output
- Example: a buffer between a gate output and several gate inputs




- The outputs of two or more gates cannot be connected to each other
  
## Three-State Buffers

- Three states?
  - 0, 1
  - Hi-Z (high-impedance)
- Three-state buffer
  - B: enable input
  - When B is 0, the output C acts like an open circuit
- Four kinds of three-state buffers




B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

 

B	A	C
0	0	0
0	1	1
1	0	Z
1	1	Z




B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

 

B	A	C
0	0	1
0	1	0
1	0	Z
1	1	Z

 
## Multiplexer Using Three-State Buffers

- 2-to-1 multiplexer
  - When  $B = 0$ , the top buffer is enabled, so  $D = A$
  - When  $B = 1$ , the lower buffer is enabled, so  $D = C$
- Two three-state buffers could be combined



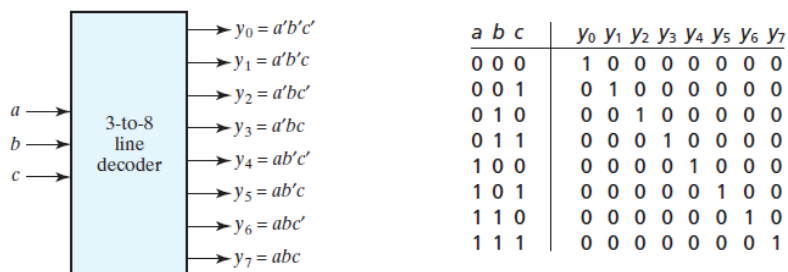
## 3-to-8 Line Decoder

- Decoder
  - Generates all of the minterms of the input variables
  - Exactly one of the output lines is 1 for each input combination
- Example: 3-to-8 line decoder



# 3-to-8 Line Decoder: Example

74LS138 (3-to-8 line decoder)

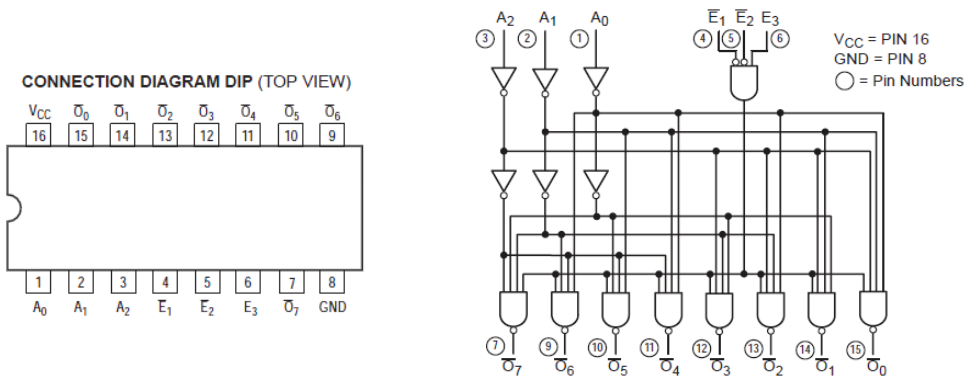


Supplementary

논리회로 9-13

# 4-to-10 Line Decoder

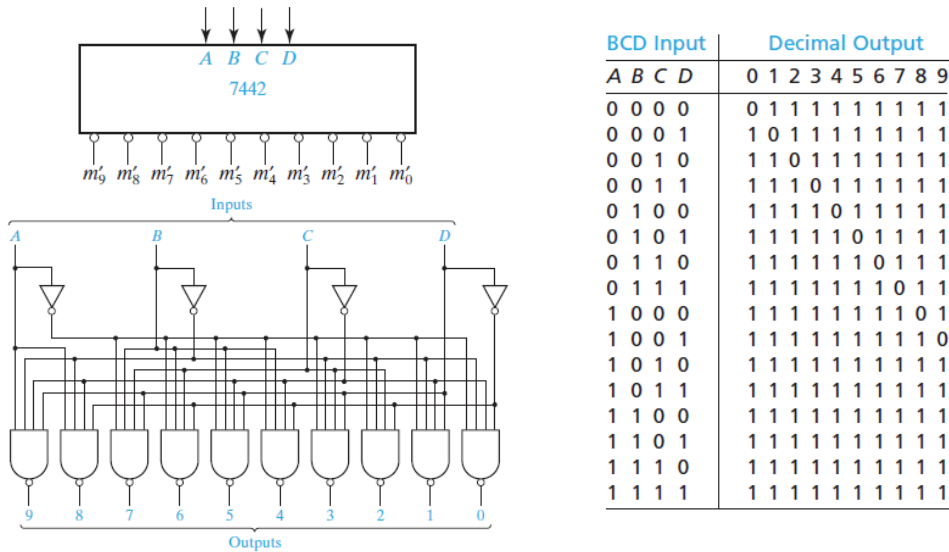- Example: 4-to-10 line decoder with inverted outputs
  - Exactly one of the output lines will be 0 for each input combination



9.4 Decoders and Encoders


논리회로 9-14

## Implementation of a 4-Variable Function (2)

### Decoder implementation

$$f_1(a, b, c, d) = m_1 + m_2 + m_4$$


$$f_2(a, b, c, d) = m_4 + m_7 + m_9$$

 

## Encoder
 
### Encoder

- Performs the inverse function of a decoder
- If input  $y_i$  is 1 and the other inputs are 0, the  $abc$  outputs represent a binary number equal to  $i$




- Only 8 input combinations are allowed



# Priority Encoder
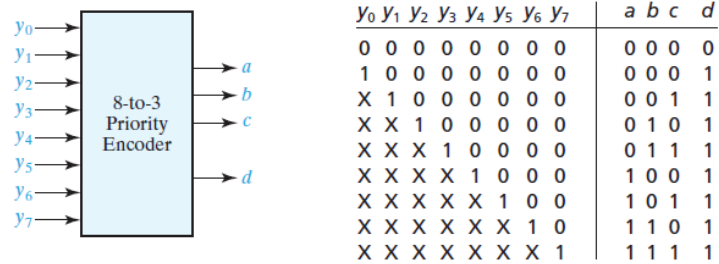
## ■ Priority?

- If only an input  $y_i$  is 1, the outputs,  $abc$  are a binary number equal to  $i$
- If more than one inputs are 1, the outputs are defined on a priority basis
- If any input is not 1,  $d$  is defined as 0, which indicates the  $abc$  output is not defined



## ■ Output $d = 0$

- If any input is not 1
- Means that the  $abc$  output is not defined


# Read-Only Memory (ROM)

## ■ ROM

- An array of semiconductor devices to store binary data
- Once binary data is stored, it can be read out whenever desired
- Stored data cannot be changed under normal operating conditions

## ■ Example: $2^3 \times 4$ ROM


- Realizes 4 functions of 3 variables

 

# Read-Only Memory (ROM)
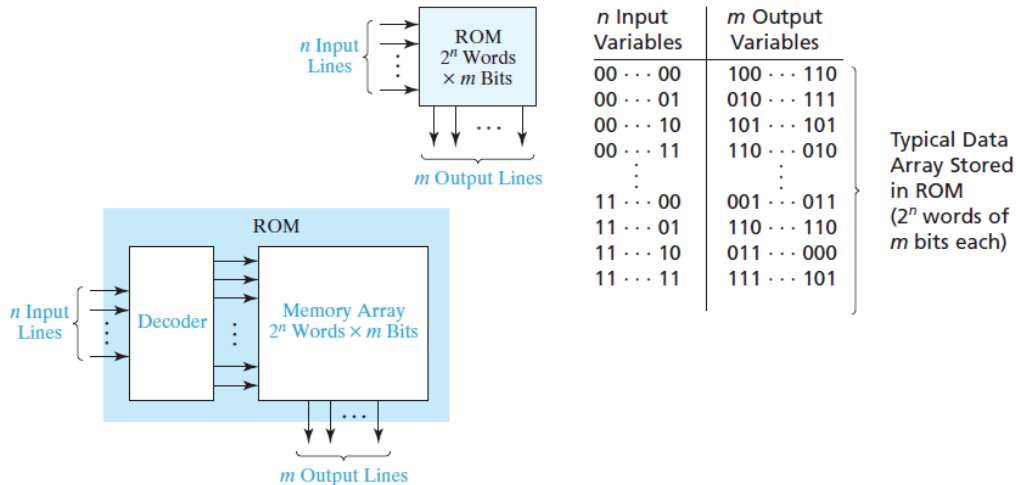
## ■ $2^n \times m$ ROM


- Can realize  $m$  functions of  $n$  variables
- Can store a truth table with  $2^n$  rows and  $m$  columns



## Implementation of a 4-Variable Function (3)

### ROM implementation

Input	Hex	ASCII Code for Hex Digit
$W X Y Z$	Digit	$A_6 A_5 A_4 A_3 A_2 A_1 A_0$
0 0 0 0	0	0 1 1 0 0 0 0
0 0 0 1	1	0 1 1 0 0 0 1
0 0 1 0	2	0 1 1 0 0 1 0
0 0 1 1	3	0 1 1 0 0 1 1
0 1 0 0	4	0 1 1 0 1 0 0
0 1 0 1	5	0 1 1 0 1 0 1
0 1 1 0	6	0 1 1 0 1 1 0
0 1 1 1	7	0 1 1 0 1 1 1
1 0 0 0	8	0 1 1 1 0 0 0
1 0 0 1	9	0 1 1 1 0 0 1
1 0 1 0	A	1 0 0 0 0 0 1
1 0 1 1	B	1 0 0 0 0 1 0
1 1 0 0	C	1 0 0 0 0 1 1
1 1 0 1	D	1 0 0 0 1 0 0
1 1 1 0	E	1 0 0 0 1 0 1
1 1 1 1	F	1 0 0 0 1 1 0


 


# Programmable Logic Devices

- Programmable Logic Device (PLD)
  - A digital IC that can be *programmed* to implement an arbitrary logic function
  - Undefined at the time of manufacture
  - Must be programmed before being used
- Some variants
  - PLA
  - PAL: special case of PLA
  - CPLD (Complex Programmable Logic Devices)
  - FPGA (Field Programmable Gate Array)
  
## Programmable Logic Array (PLA)

- PLA with  $n$  inputs and  $m$  outputs



- Example: PLA with 3 inputs and 4 outputs
  - 5 product terms are *programmed* with 3 inputs
  - 4 outputs are *programmed* with the 5 product terms

# Programmable Array Logic (PAL)

- PAL
  - AND array is programmable
  - OR array is fixed

