

## Unit 7

# Multi-level Gate Circuits

## NAND and NOR Gates

Logic Circuits (Spring 2022)


### Multi-level Circuits

---

- Number of *levels* of gates
  - The maximum number of gates cascaded in series between a circuit input and the output
  - Inverters are normally NOT counted  $\Leftarrow$  most inputs are driven from flip-flop outputs, and the complements are provided with its original value
- AND-OR circuits: a two-level circuit
  - A level of **AND gates**
  - Followed by an **OR gate** at the output
- OR-AND circuit: a two-level circuit
- OR-AND-OR circuit: a three-level circuit
  - A level of **OR gates**
  - Followed by a level of **AND gates**
  - Followed by an **OR gate** at the output


## Example 1: Four-level Design

$$Z = (AB + C)(D + E + FG) + H$$

 
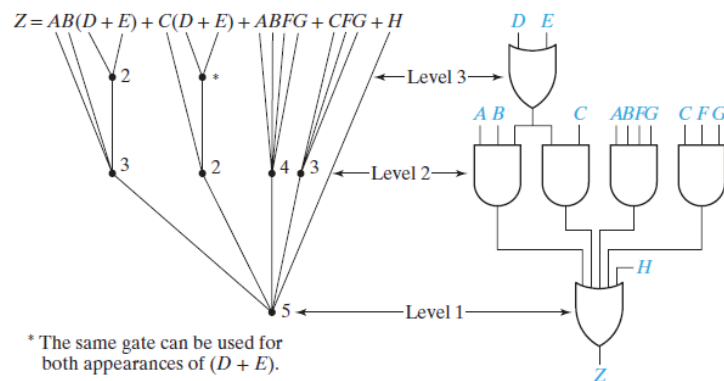
## Example 1: Three-level Design

$$Z = AB(D + E) + C(D + E) + ABFG + CFG + H$$




## Example 2: AND-OR Circuit

$$f(a, b, c, d) = \Sigma m(1, 5, 6, 10, 13, 14)$$

$$f = d'c'd + bc'd + bcd' + acd'$$

ab \ cd	00	01	11	10
00	0	0	0	0
01	1	1	1	0
11	0	0	0	0
10	0	1	1	1

 


# of gate inputs =

## Example 2: OR-AND-OR Circuit

$$f(a, b, c, d) = \Sigma m(1, 5, 6, 10, 13, 14)$$

$$f = d'c'd + bc'd + bcd' + acd'$$

$$f = c'd(a' + b) + cd'(a + b)$$

 


# of gate inputs =

## Example 2: OR-AND Circuit

$$f(a, b, c, d) = \Sigma m(1, 5, 6, 10, 13, 14)$$

$$f' = c'd' + ab'c' + cd + a'b'c$$
 
$$f = (c + d)(a' + b + c)(c' + d')(a + b + c')$$



# of gate inputs =

## Example 2: AND-OR-AND Circuit


$$f(a, b, c, d) = \Sigma m(1, 5, 6, 10, 13, 14)$$

$$f' = c'd' + ab'c' + cd + a'b'c$$

$$f = (c + d)(a' + b + c)(c' + d')(a + b + c')$$

$$f = [c + d(a' + b)][c' + d'(a + b)]$$

$$f = (c + a'd + bd)(c' + ad' + bd')$$

 

# of gate inputs =

## NAND Gates


### ■ NAND Gate

- Equivalent to an AND gate followed by an inverter
- AND-NOT gate

### ■ $n$ -input NAND gate's output

$$F = (X_1 X_2 \dots X_n)' = X_1' + X_2' + \dots + X_n'$$

### ■ Symbols

 

## NOR Gates


### ■ NOR Gate

- Equivalent to an OR gate followed by an inverter
- OR-NOT gate

### ■ $n$ -input NOR gate's output

$$F = (X_1 + X_2 + \dots + X_n)' = X_1' X_2' \dots X_n'$$


### ■ Symbols

 

# Functionally Complete Operations & Gates

 
## ■ Functionally complete set of operations

- A set of logic operations is said to be *functionally complete* if any Boolean function can be expressed in terms of this set of operations
- A simple example set: { AND, OR, NOT }
- Another example set: { AND, NOT }


 
## ■ Functionally complete gate

- If a single gate forms a functionally complete set by itself, then any switching function can be realized using only gates of that type
- Example: NAND




7.2 NAND and NOR Gates


논리회로 7-11

# Alternative Gate Symbols

## ■ Inverters

 


## ■ AND, OR, NAND, NOR

 

7.5 Circuit Conversion Using Alternative Gate Symbols

논리회로 7-12
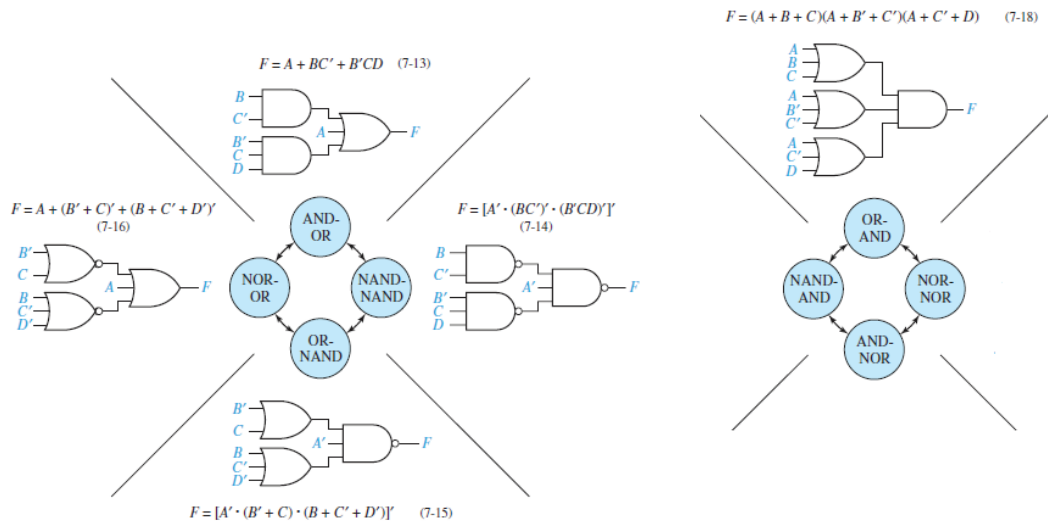
# Eight Basic Forms for Two-Level Circuits






7.3 Design of Two-Level NAND- and NOR-Gate Circuits

논리회로 7-13

## NAND Gate Circuit Conversion
   
### ■ NAND gates $\Rightarrow$ AND-OR network




7.5 Circuit Conversion Using Alternative Gate Symbols

논리회로 7-14

 
## NAND Gate Circuit Conversion

- Two-level AND-OR network  $\Rightarrow$  NAND gates
  - Find a minimum sum-of-products expression
  - Draw the corresponding two-level AND-OR circuit
  - Replace all gates with NAND gates leaving the gate interconnection unchanged
  - If the output gate has any single literals as inputs, complement these literals



 
## NAND Gate Circuit Conversion


- AND-OR network  $\Rightarrow$  NAND gates



(a) AND-OR network

 

(b) First step in NAND conversion

 

(c) Completed conversion




## NOR Gate Circuit Conversion


- Two-level OR-AND network  $\Rightarrow$  NOR gates
  - Find a minimum product-of-sums expression
  - Draw the corresponding two-level OR-AND circuit
  - Replace all gates with NOR gates leaving the gate interconnection unchanged
  - If the output gate has any single literals as inputs, complement these literals
 
## NOR Gate Circuit Conversion

- OR-AND network  $\Rightarrow$  NOR gates



(a) Circuit with OR and AND gates

 

(b) Equivalent circuit with NOR gates

## Multi-level Design Using NAND & NOR Gates

- Procedure to design a multi-level NAND gate circuits
  - Simplify the switching function to be realized
  - Design a multi-level circuit of AND & OR gates. The output gate must be OR. AND gate outputs cannot be used as AND gate inputs. OR gate outputs cannot be used as OR gate inputs
  - Number the levels starting with the output gate as level 1. Replace all gates with NAND gates, leaving all interconnection between gates unchanged.
  - Leave the inputs to level 2, 4, 6, ... unchanged. Invert any literals which appear as inputs to levels 1, 3, 5, ...

.... – AND – OR – AND – OR

4      3      2      1

## Multi-level Design Using NAND & NOR Gates

$$F_1 = a'[b' + c(d + e') + f'g'] + hi'j + k$$

