### Unit 16

# Sequential Circuit Design

Logic Circuits (Spring 2022)

# BCD to Excess-3 Code Converter


- Specification
  - Add three to a binary-coded-decimal digit in the range 0 to 9

X Input				Z				
				Output				
(BCD)			(excess-3)					
t <sub>3</sub>	$t_2$	$t_1$	t <sub>0</sub>	t <sub>3</sub>	t <sub>2</sub>	t <sub>1</sub>	$t_0$	
0	0	0	0	0	0	1	1	
0	0	0	1	0	1	0	0	
0	0	1	0	0	1	0	1	
0	0	1	1	0	1	1	0	
0	1	0	0	0	1	1	1	
0	1	0	1	1	0	0	0	
0	1	1	0	1	0	0	1	
0	1	1	1	1	0	1	0	
1	0	0	0	1	0	1	1	
1	0	0	1	1	1	0	0	

16.2 Design Example – Code Converter

# BCD to Excess-3 Code Converter

#### ■ State diagram

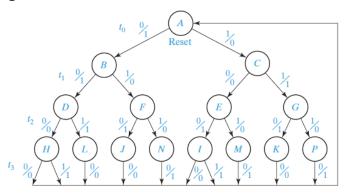

16.2 Design Example – Code Converter

논리회로 16-3

# BCD to Excess-3 Code Converter

#### State table

	Input Sequence Received				Prese	nt
	(Least Significant	Present	Next St	ate	Output	(Z)
Time	Bit First)	State	X = 0	1	X = 0	1
$t_0$	reset	Α	В	C	1	0
t <sub>1</sub>	0	В	D	F	1	0
	1	C	E	G	0	1
	00	D	Н	L	0	1
4	01	E	1	M	1	0
$t_2$	10	F	J	Ν	1	0
	11	G	K	P	1	0
	000	Н	Α	Α	0	1
	001	1	A	A	0	1
	010	J	A	_	0	_
4	011	K	A	_	0	_
$t_3$	100	L	A	_	0	_
	101	M	A	_	1	_
	110	N	A	_	1	_
	111	Р	Α	-	1	_


#### Reduced state table

		Next		Present	
	Present	State		Output (Z	
Time	State	X = 0	1	X = 0	1
<b>t</b> <sub>0</sub>	Α	В	C	1	0
t <sub>1</sub>	В	D	Ε	1	0
	С	E	E	0	1
t <sub>2</sub>	D	Н	Н	0	1
	Ε	Н	M	1	0
t <sub>3</sub>	Н	Α	Α	0	1
	M	A	_	1	_

16.2 Design Example – Code Converter

### BCD to Excess-3 Code Converter

Assignment map

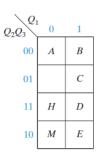

■ Transition table


		$Q_1^+Q_2^+Q_3^+$		Z	
	$Q_1Q_2Q_3$	X = 0	<i>X</i> = 1	X = 0	<i>X</i> = 1
A	000	100	101	1	0
В	100	111	110	1	0
C	101	110	110	0	1
D	111	0 1 1	0 1 1	0	1
E	110	0 1 1	010	1	0
Н	0 1 1	000	000	0	1
Μ	0 1 0	000	XXX	1	X
-	0 0 1	xxx	XXX	X	X

16.2 Design Example - Code Converter

논리회로 16-5

### BCD to Excess-3 Code Converter


Next state and output maps

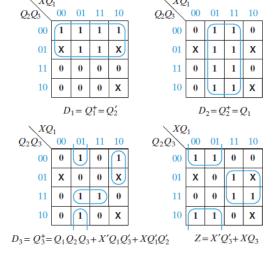

16.2 Design Example - Code Converter

# BCD to Excess-3 Code Converter

### ■ Logic diagram

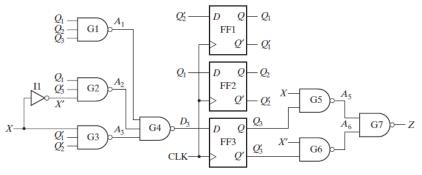

16.2 Design Example – Code Converter