

Unit 5

Karnaugh Maps

Logic Circuits (Spring 2022)

Minimum Sum-of-Products

- A sum of product terms is a *minimum* SOP expression
 - It has a minimum number of *terms*
 - It has a minimum number of *literals*, for all those expressions with the same minimum number of terms
- Minimum two-level gate circuit
 - It has a minimum number of gates and gate inputs
 - A minimum SOP \Rightarrow a minimum 2-level circuit
- How to find a minimum sum-of-products
 - Combine terms by using the uniting theorem $XY + XY' = X$
 - Eliminate redundant terms by using the consensus theorem or other theorems
 - Eliminate literals by using the theorem $X + X'Y = X + Y$

Minimum Sum-of-Products: Example

■ Example: $F(a, b, c) = \sum m(0, 1, 2, 5, 6, 7)$

- Minimum SOP expression: the first case

$$F = a'b'c' + a'b'c + a'bc' + ab'c + abc' + abc$$

$$= a'b' + b'c + bc' + ab$$

- Minimum SOP expression: the second case

$$F = a'b'c' + a'b'c + a'bc' + ab'c + abc' + abc$$


$$= a'b' + bc' + ac$$

- Combining terms in a different way may lead to a different minimum expressions

Karnaugh Map

■ Karnaugh map

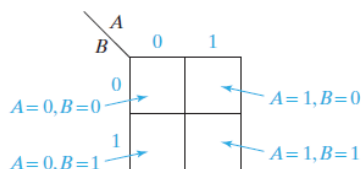- A systematic way of simplifying switching functions
- Specifies the value of the function for every combination of values of the independent variables
- Each 1 on the map corresponds to a minterm



		A		0	1
		BC		00	01
ABC = 001, F = 0	00	0	1		
	01	0	0		
	11	1	0		
	10	1	1		

ABC = 110, F = 1

F

Two-Variable Karnaugh Map

■ Variable and value

- The value of a variable A is listed on the top
- The value of the other B is listed on the side

■ Truth table \Rightarrow Karnaugh map

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

		A	
		0	1
B	0	1	0
	1	1	0

		A	
		0	1
B	0	1	0
	1	1	0

$F = A'B' + A'B$

		A	
		0	1
B	0	1	0
	1	1	0

$A'B' + A'B = A'$
 $F = A'$

■ Properties of Karnaugh map

- A square represents a minterm
- Minterms in adjacent squares differ in only one variable
 \Rightarrow the minterms can be combined
- Product terms are represented by one or more squares

Three-Variable Karnaugh Map

■ Variable and value

- The value of a variable A is listed on the top
- The values of the other B and C are listed on the side

■ Truth table \Rightarrow Karnaugh map

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		A	
		0	1
BC	00	0	1
	01	0	0
11	11	1	0
	10	1	1


$ABC = 001, F = 0$

$ABC = 110, F = 1$

F

Drawing a Karnaugh Map

■ Locations of minterms

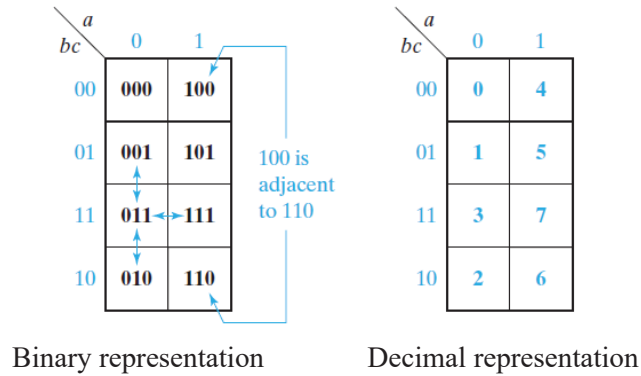

- Minterm $ab'c'$ is adjacent to minterm $a'b'c'$, $ab'c$, and abc'
- Minterm m_4 is adjacent to minterm m_0 , m_5 , and m_6


Drawing a Karnaugh Map

- Mapping minterm and maxterm expressions on Karnaugh map
- Example: $F(a, b, c) = \sum m(1, 3, 5) = \prod M(0, 2, 4, 6, 7)$

$a \backslash bc$	0	1
00	0 0	0 4
01	1 1	1 5
11	1 3	0 7
10	0 2	0 6


Drawing a Karnaugh Map

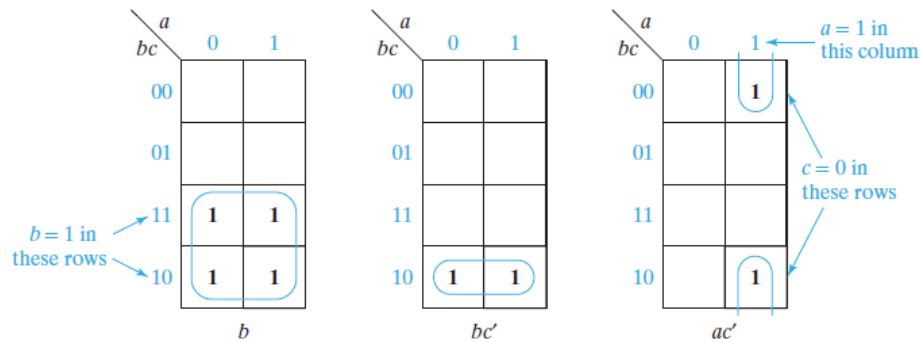- Plotting product terms
- Example: b , bc' , ac'




Drawing a Karnaugh Map

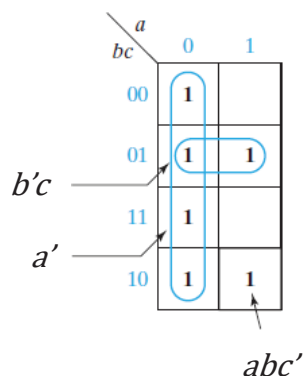- Plotting an expression in algebraic form
- Example: $f(a, b, c) = abc' + b'c + a'$




Veitch Diagram

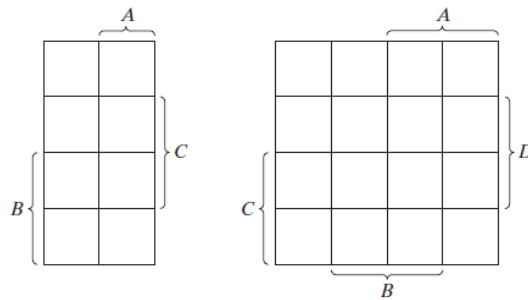- Other forms of Karnaugh maps
- Using different labeling
 - $A = 1$ for the half of the map labeled A
 - $A = 0$ for the other half




Utilizing a Karnaugh Map

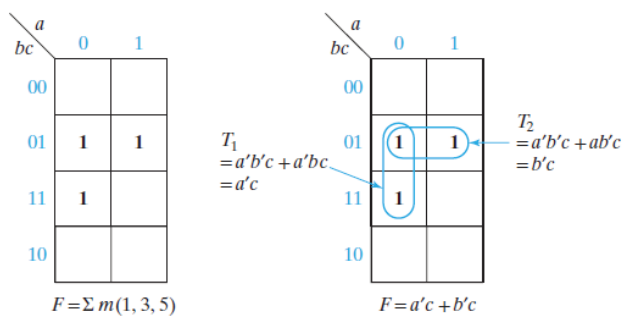- Simplifying an expression
- Example: $F = \sum m(1, 3, 5) = a'c + b'c$




Utilizing a Karnaugh Map

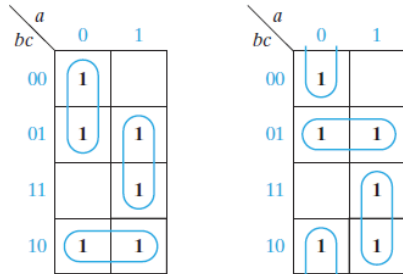- Simplification based on Karnaugh map
- Example: $F = \Sigma m(0, 1, 2, 5, 6, 7)$



Utilizing a Karnaugh Map

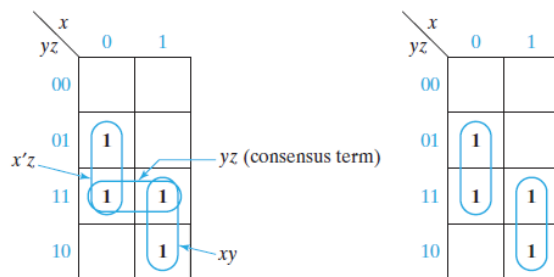- Consensus theorem
- Example: $xy + x'z + yz = xy + x'z$




Four-Variable Karnaugh Map

■ Location of terms


$AB \backslash CD$	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

Karnaugh Map

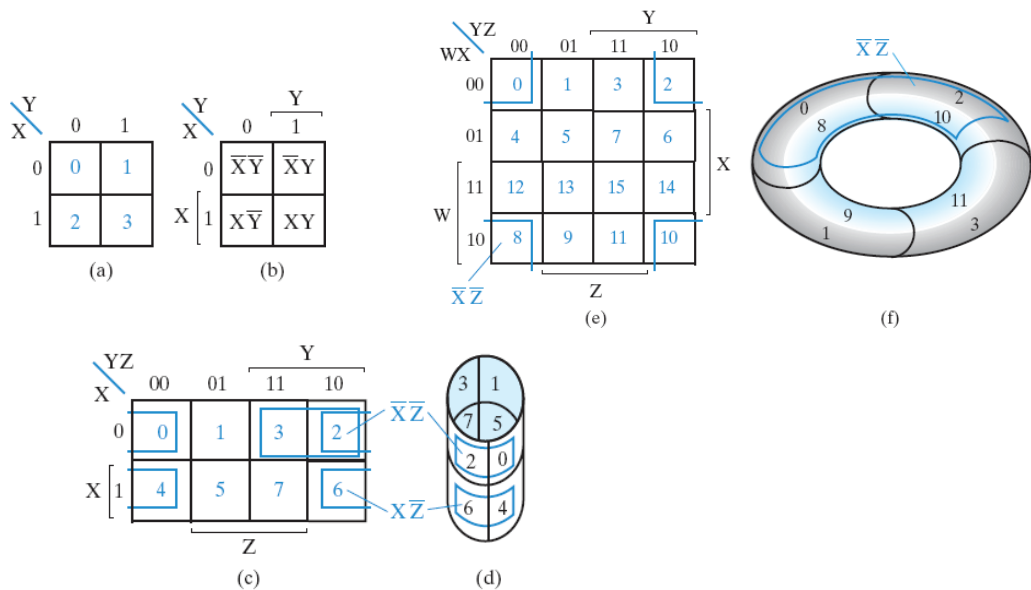


Four-Variable Karnaugh Map

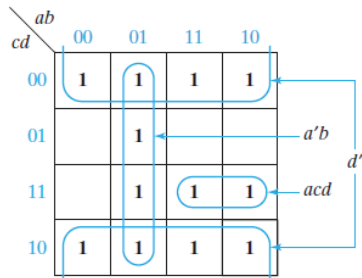- Plotting a four-variable function
- Example: $acd + a'b + d'$




Four-Variable Karnaugh Map

- Simplifying a four-variable expression

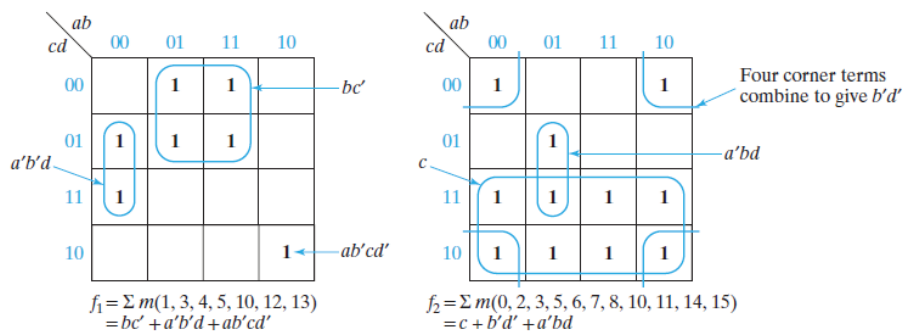

Four-Variable Karnaugh Map

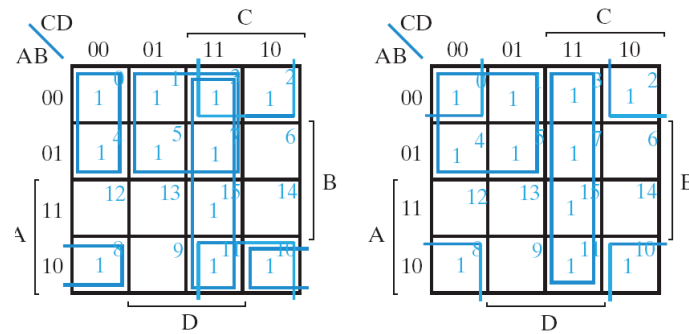
- Simplifying a four-variable expression
- Example: $A'C'D' + A'D + B'C + CD + AB'D'$



- Minimum sum-of-product expression: $A'C' + CD + B'D'$

Four-Variable Karnaugh Map

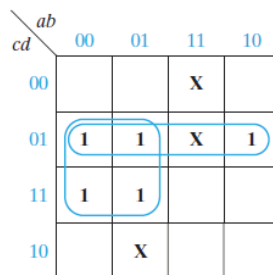- Expressions with “don’t care”
 - “don’t care” terms are noted as X’s



Four-Variable Karnaugh Map

- Application: SOP \Rightarrow POS form

- Example

$$f = x'z' + wyz + w'y'z' + x'y$$

$$f' = y'z + wxz' + w'xy$$

$$f = (y + z')(w' + x' + z)(w + x' + y')$$

wx \ yz	00	01	11	10
00	1	1	0	1
01	0	0	0	0
11	1	0	1	1
10	1	0	0	1

Prime Implicants

- *Implicant*

- A product term of an expression
- If the product term is equal to 1, the expression is also equal to 1

- *Prime implicant*

- An implicant that can not be combined with another implicant
- The implicant is no longer an implicant if any literal is deleted from it

- Example


- Prime implicant: ac' , $a'b'c$, $a'cd'$
- Non prime implicant: abc' , $ab'c'$, $a'b'c'd'$

- A SOP expression containing a non-prime implicant term cannot be minimum

cd \ ab	00	01	11	10
00	1		1	1
01			1	1
11	1			
10	1	1		


Prime Implicants: Example

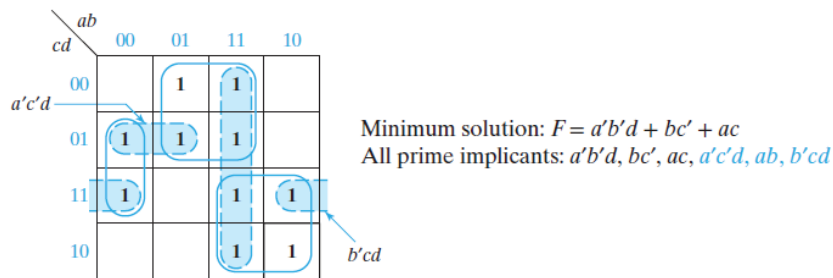- All of the prime implicants are generally not needed
 \Rightarrow The minimum solution may not include all prime implicants
- Example



Essential Prime Implicant

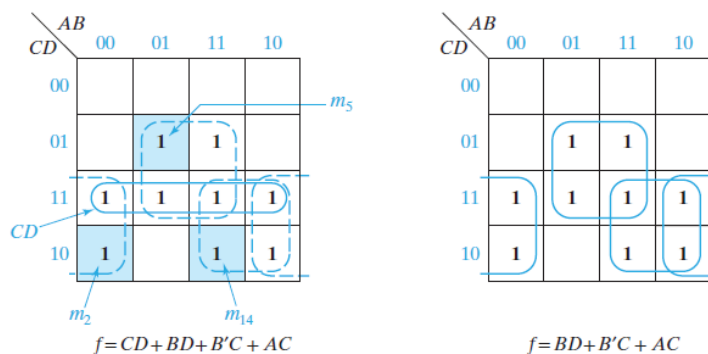- Covering minterms
 - Some minterms can be covered by only a single prime implicant




- Essential prime implicant
 - A prime implicant that covers a minterm that any other prime implicant could not cover
 - Essential prime implicants must be included in the minimum SOP

Essential Prime Implicants: Example

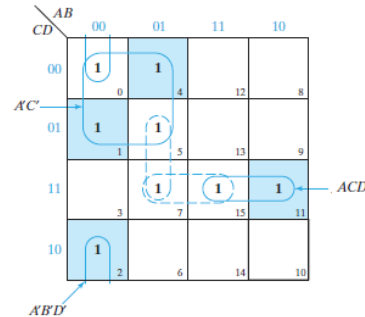- Example: $F = \sum m(0, 1, 2, 4, 5, 7, 11, 15)$

- Prime implicants

- Essential prime implicants:
 $A'C$, $A'B'D'$, ACD



- Minimum sum-of-product expression

$$A'C + A'B'D' + ACD + \left\{ \begin{array}{c} A'BD \\ \text{or} \\ BCD \end{array} \right\}$$

Procedure to Obtain a Minimum SOP

1. Choose a minterm (a 1) which has not yet been covered.
2. Find all 1's and X's adjacent to that minterm. (Check the n adjacent squares on an n -variable map.)
3. If a single term covers the minterm and all of the adjacent 1's and X's, then that term is an essential prime implicant, so select that term. (Note that "don't-care" terms are treated like 1's in steps 2 and 3 but not in step 1.)
4. Repeat steps 1, 2, and 3 until all essential prime implicants have been chosen.
5. Find a minimum set of prime implicants which cover the remaining 1's on the map. (If there is more than one such set, choose a set with a minimum number of literals.)