

Unit 12

Registers and Counters


Logic Circuits (Spring 2022)

Registers

- *Register*
 - A group of flip-flops with a common clock input
 - Commonly used to store and shift binary data
- *Shift register*
 - A bit is shifted out one end, and it may be lost or shifted back in the other end
 - The serial input is loaded into the first or the last flip-flop
- *Accumulator*
- *(Binary) Counter*
 - A circuit that cycles through a fixed sequence of states
 - Usually constructed from two or more flip-flops which change states in a prescribed sequence when input pulses are received

4-Bit D Flip-Flop Register

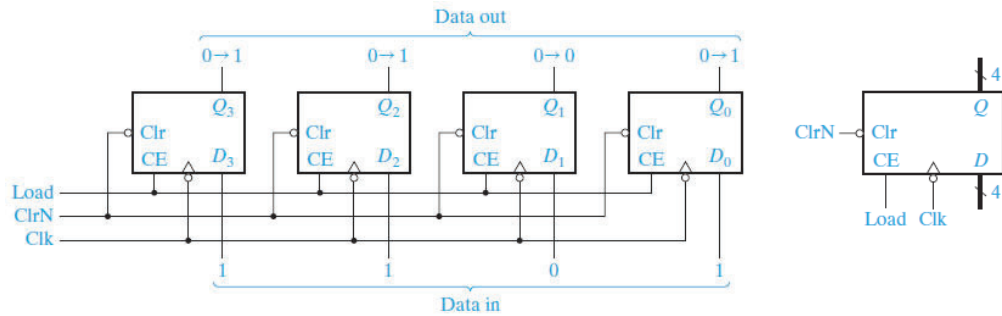
- 4-bit register
 - Each flip-flop stores one bit of information
 - 4-bit register stores 4 bits of information



- Signals and operations
 - When asynchronous clear signal(ClrN) = 0, the Q output will become 0
 - When Load = 1, the Clock Enable(CE) becomes 1 and thus the data applied to D inputs will be loaded in the flip-flops on falling edge
 - When Load = 0, the clock is disabled and the register holds its data

Shift Register

 
- *Shift register*
 - A register to store binary data
 - The data stored in a shift register can be shifted to the left or right when a shift signal is applied
 - Bits shifted out one end may be lost or shifted back in the other end



- Signals
 - Shifting occurs on the rising clock edge when Shift = 1
 - No shifting occurs and the data is unchanged when Shift = 0

Shift Register

■ Timing diagram

 


- Serial input(SI) is loaded into the first flip-flop(Q_3)
- The output of the first flip-flop(Q_3) is loaded into the second flip-flop
-

(Serial-In, Serial-Out) Shift Register


■ 8-bit *serial-in, serial-out* shift registers

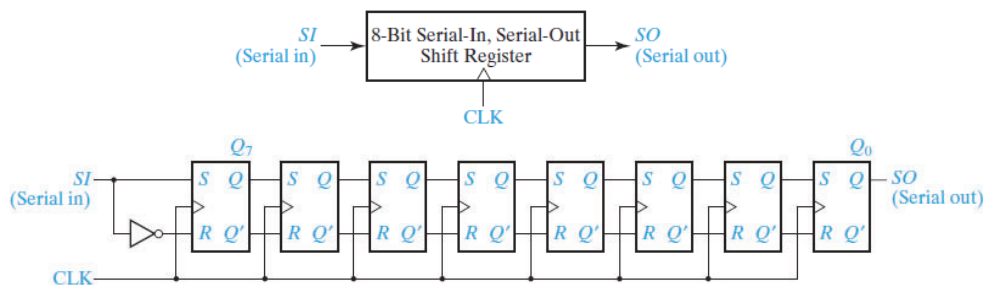- Serial in: data is shifted into the first flip-flop one bit at a time,
- Serial out: data can only be read out of the last flip-flop and the outputs from the other flip-flops are not connected to terminals
- Cannot load data in parallel




(Serial-In, Serial-Out) Shift Register

■ Timing diagram

 


Universal Shift Register

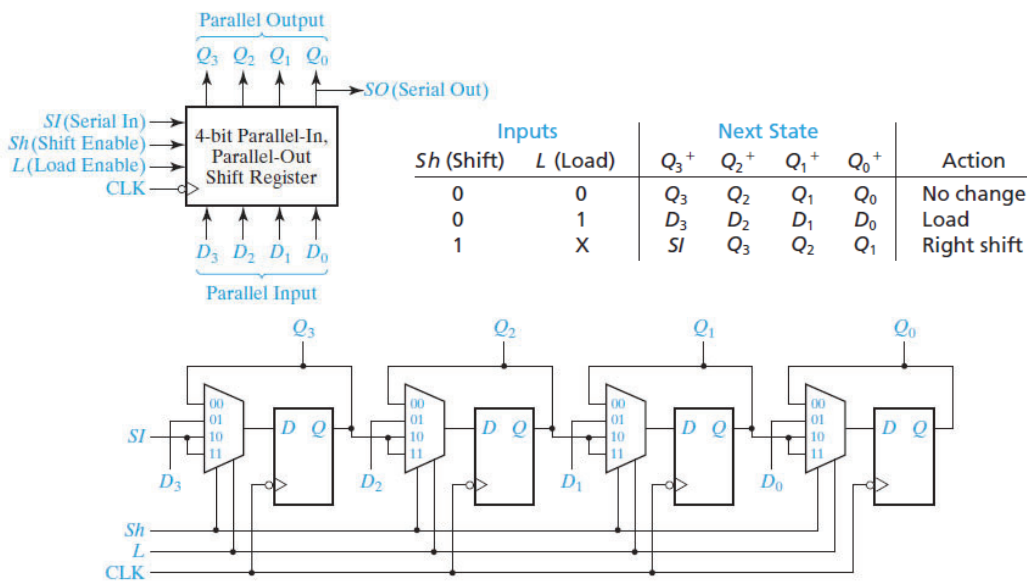■ 4-bit parallel-in, parallel-out shift registers



Universal Shift Register


■ Timing diagram

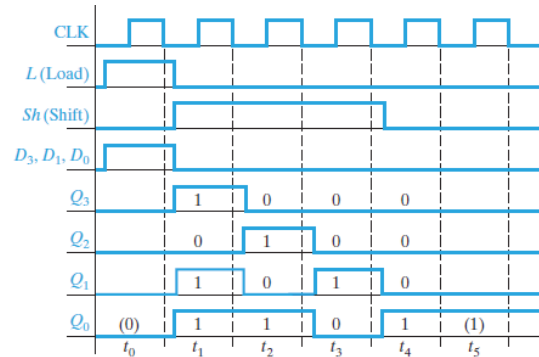

Parallel Adder with Accumulator

■ Accumulator

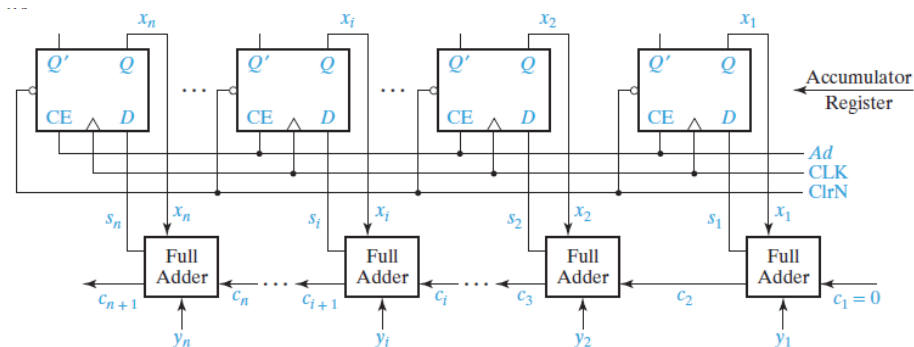- Register in which intermediate arithmetic and logic results are stored
- Example: a number stored in an accumulator is added to a second number in another register




■ n -bit accumulator can be combined with n full adders

- $s_i \leftarrow x_i + y_i + c_i$

Parallel Adder with Accumulator

■ Typical adder cell with multiplexer

 

■ Two operations

- Accumulator could be loaded with the given number (when $Ld = 1$)
- Accumulator could store the sum with the given number (when $Ad = 1$, and $Ld = 0$)

Binary Counter

■ Synchronous counters

- The operation of the flip-flops is synchronized by a common clock pulse
- When several flip-flops must change state, the state changes occur simultaneously.


■ Ripple counters

- The state change of one flip-flop triggers another flip-flop

Johnson Counters



■ Ring counter

- A shift register with feedback

 

■ Johnson counter

  - A shift register with inverted feedback
- Also called as a *twisted ring counter*



Binary (Up) Counter with D Flip-flops

■ Transition of 3-bit counter


- 000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000

■ Transition table (Next state table)

Present State			Next State		
C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Binary (Up) Counter with D Flip-flops

■ Karnaugh maps for D_C , D_B , and D_A

 

■ Flip-flop input equations


$$D_A = A^+ = A'$$

$$D_B = B^+ = BA' + B'A = B \oplus A$$

$$D_C = C^+ = C'BA + CB' + CA' = C'BA + C(BA)' = C \oplus BA$$


Binary (Up) Counter with D Flip-flops

■ Logic diagram

 

Binary Up-Down Counter

■ Transition graph and table

 

CBA	$C^+B^+A^+$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

■ Flip-flop input equations


$$D_A = A^+ = A \oplus (U + D)$$

$$D_B = B^+ = B \oplus (UA + DA')$$

$$D_C = C^+ = C \oplus (UBA + DB'A')$$


Binary Up-Down Counter

■ Logic diagram

 

Binary Counter for Other Sequences

 - An example counter
 - 000 → 100 → 111 → 010 → 011
- Transition graph and table




C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	1	0	0
0	0	1	–	–	–
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	–	–	–
1	1	0	–	–	–
1	1	1	0	1	0

- Incompletely specified transition table

Binary Counter for Other Sequences

 - Karnaugh maps for D flip-flop implementation




$$D_C = C^+ = B' \quad D_B = B^+ = C + BA'$$

$$D_A = A^+ = CA' + BA' = A'(C + B)$$

Binary Counter for Other Sequences

 ■ Logic diagram for D flip-flop implementation



Self-Starting Counter

- Problems with incompletely specified transition graph
 - The initial states may be unpredictable when the power is turned on
 - What happens if the state becomes unspecified
 - Example: state 001 ($C = 0, B = 0, A = 1$)
- *Self-starting counter*
 - Don't care states eventually lead into the main counting sequence
 - Example: state 001 goes to 111

