

Unit 11

Latches and Flip-Flops

Logic Circuits (Spring 2022)

"Memory" Devices

- *Sequential* switching circuits
 - The output depends not only on *the present input* but also on *the past sequence of inputs*
 - The circuits must be able to “remember” something about the past history of the inputs in order to produce the present output
- *Latches and flip-flops*
 - Commonly used memory devices in sequential circuits
 - Assume one of two stable output states
 - Have one or more inputs that can cause the output state to change

Latch vs. Flip-Flop

- Latch
 - A memory element that has no clock input
 - Each latch works *independently* with respect to timing
 - Flip-flop
 - A memory element that has a clock input
 - The operation of all flip-flops are *synchronized* by a common clock or pulse generator
 - The flip-flops can only change output in response to a clock input, not data inputs
 - Synchronous circuits
 - The changes in the state of memory devices are synchronized by a clock signal
 - Nearly all digital circuits are fully synchronous
- cf.* Asynchronous circuits

Feedback

- The output of one of the gates is connected back into the input of another gate in the circuit so as to form a closed loop
- A feedback loop with an inverter




- A feedback loop with two inverters



S-R Latch (Set-Reset Latch)


- A feedback loop with two NORs

 

- Initially, $P=1, Q=0$
- $S=0, R=0$
 - The circuit remains stable with $P=1$ and $Q=0$
- $S=1, R=0$
 - P will become 0, and then Q will become 1
- $S=0, R=0$ (S is changed back to 0)
 - The circuit will not change the state

S-R Latch (Set-Reset Latch)


- Now $P=0, Q=1$

 


- $S=0, R=0$
 - The circuit remains stable with $P=0$ and $Q=1$
- $S=0, R=1$
 - Q will become 0, and then P will become 1
- $S=0, R=0$ (R is changed back to 0)
 - The circuit will not change the state
- Characteristics of S-R latch
 - The output depends not only on the present inputs, but also on the past sequence of inputs
 - P and Q are always complements $\Rightarrow P = Q'$

S-R Latch (Set-Reset Latch)

■ Cross-coupled form of S-R latch

 


■ Timing diagram

 

S-R Latch (Set-Reset Latch)

 - $R=S=1$ is not allowed
 - Both P and Q are all 0's $\Rightarrow P \neq Q'$
 - If both inputs change 1 to 0 simultaneously, the latch may continue to oscillate



S-R Latch (Set-Reset Latch)

- *Present state* $Q(t)$
 - The state of the Q output at the time any input signal changes
- *Next state* $Q(t+\varepsilon)$ (or $Q(t+1)$)
 - The state of the Q output after the latch or flip-flop has reached to the input change and stabilized
- *Next-state equation*

Present State Q	Next State Q^+			
	SR 00	SR 01	SR 11	SR 10
0	0	0	0	1
1	1	0	0	1

$$Q(t + \varepsilon) = R(t)'[S(t) + Q(t)]$$

$$= R(t)'S(t) + R(t)'Q(t)$$

$$Q^+ = R'S + R'Q$$

The stable states are circled

S-R Latch (Set-Reset Latch)

- *Characteristic equation*
 - Takes into account any disallowed input equation ($S=R=1$)
 - Not necessarily the same as the next-state equation

Present State Q	Next State Q^+			
	SR 00	SR 01	SR 11	SR 10
0	0	0	X	1
1	1	0	X	1

$S \backslash RQ$		
	0	1
00	0	1
01	1	1
11	0	X
10	0	X


S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Inputs not allowed
1	1	1	

$$Q^+ = S + R'Q \quad (SR = 0)$$


$\bar{S}\text{-}\bar{R}$ Latch using NAND Gates

- Alternative form of S-R Latch
 - Uses NAND gates

 - Circuit representation
 - Set Q to 1 when $\bar{S} = 0$
 - Reset Q to 0 when $\bar{R} = 0$



- Symbol representation

 


$\bar{S}\text{-}\bar{R}$ Latch using NAND Gates

- Truth table representation

\bar{S}	\bar{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	} Inputs not allowed
0	0	1	

Gated S-R Latches

 - *Gate or enable* input
 - *Gated latches* have an additional input called the *gate* or *enable* input
 - When the gate input is inactive, the state of the latch cannot change
 - When the gate input is active, the latch operates in an ordinary way
- NAND-gate gated S-R latch



Gated S-R Latches

- Next state table

Present State Q	Next State Q^+							
	$G = 0$				$G = 1$			
	SR 00	SR 01	SR 11	SR 10	SR 00	SR 01	SR 11	SR 10
0	0	0	0	0	0	0	1	1
1	1	1	1	1	1	0	1	1


- Next-state equation

$$Q^+ = SG + Q(R' + G')$$


GQ	SR			
	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	0	1	1
10	0	0	1	1
Q^+				

Gated D Latch

 - Transparent latch
 - Q becomes equal to D while G is active



- Timing diagram

 

Gated D Latch

- Next-state equation / Characteristic equation


G	D	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

GD	00	01	11	10
Q				
0	0	0	1	0
1	1	1	1	0

$$Q^+ = G'Q + GD$$

Problems with the Latches

- Example circuit

 



- The output changes any time
- The latch takes its input any time

Flip-Flops

- *Flip-flop*
 - The **outputs** only change on a clock edge
- *Edge-triggered flip-flop*
 - The flip-flop take **inputs** on a clock edge
 - The **inputs** to the flip-flop only need to be stable for a short period of time around the clock edge
- *Master-slave flip-flop*
 - The flip-flop takes **inputs** during the clock period


Rising Edge-Triggered D Flip-Flop

  - The output can change on a 0 to 1 transition on the clock input
- Construction from two gated D latches



Rising edge-triggered =
positive edge-triggered

- Timing diagram

 



Falling Edge-Triggered D Flip-Flop

- The output can change on a 1 to 0 transition on the clock input
- Truth table representation

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1

- Characteristic equation
 $Q^+ = D$


- Timing diagram

  


Falling edge-triggered =
negative edge-triggered

S-R Flip-Flop


Symbolic representation

 

Implementation with two latches

 

Timing diagram

 

Characteristic equation


$$Q^+ = S + R'Q \quad (SR = 0)$$

11.5 S-R Flip-Flop


논리회로 11-21

J-K Flip-Flop


Symbolic representation

 

Implementation with two latches

 

Timing diagram

 

Characteristic equation

$$Q^+ = JQ' + K'Q$$


J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

11.6 J-K Flip-Flop


논리회로 11-22

T Flip-Flop


Symbolic representation

 

Conversion of J-K/D to T

 

Timing diagram

 

Characteristic equation

$$Q^+ = T \oplus Q = TQ' + T'Q$$

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic Equations (Summary)


- Procedures to find a characteristic equation
 - Make a truth table that gives the next state (Q^+) as a function of the present state (Q) and the inputs. Any illegal input combinations should be treated as don't-cares.
 - Plot a map for Q^+ and read the characteristic equation from the map

■ Characteristic equations: Summary

$Q^+ = S + R'Q$ ($SR = 0$)	(S-R flip-flop)
$Q^+ = GD + G'Q$	(gated D latch)
$Q^+ = D$	(D flip-flop)
$Q^+ = D \cdot CE + Q \cdot CE'$	(D-CE flip-flop)
$Q^+ = JQ' + K'Q$	(J-K flip-flop)
$Q^+ = T \oplus Q = TQ' + T'Q$	(T flip-flop)

Setup and Hold Times

 - Timing constraints of a flip-flop
 - A flip-flop changes state only on the active edge of the clock
 - The D input to an edge-triggered flip-flop *must* be held at a constant value for a period of time *before* and *after* the active edge of the clock



Propagation time (t_p):

the amount of time from the clock edge to the output change

Setup time (t_{su}):



the amount of time that D must be stable before the active edge

Hold time (t_h):


the amount of time that D must hold the same value after the active edge

Minimum Clock Period

  
- Why minimum clock period?
- Example case
 - Propagation delay of an inverter: 2 ns
 - Propagation delay of a flip-flop: 5 ns
 - Setup time of a flip-flop: 3 ns



Setup time not satisfied

 


Setup time satisfied

 

Minimum clock period = 10 ns

D Flip-Flop with Clock Enable

 
- How to hold existing data with changing data inputs
 - Even though the data input to the flip-flop may be changing, we want some flip-flops to hold existing data
- One solution




- Two potential problems with the above solution
 - Gate delay may cause the clock to arrive at different times
 - The flip-flop may trigger due to the change in En instead of the clock

D Flip-Flop with Clock Enable

- Symbolic representation

 

- Implementation using a MUX

 

- Characteristic equation


$$Q^+ = D = Q \cdot CE' + D_{in} \cdot CE$$

D Flip-Flop with Clear and Preset

■ Additional inputs

- Can be used to set the flip-flops to an initial state independent of the clock
- Asynchronous Clear (ClrN)
- Asynchronous Preset (PreN)

■ Symbolic representation

 

Ck	D	PreN	ClrN	Q ⁺
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)

D Flip-Flop with Clear and Preset

■ Timing diagram

