

## Unit 13

# Analysis of Clocked Sequential Circuits

Logic Circuits (Spring 2022)


## Example: Sequential Parity Checker

### ■ (Odd) Parity bit

- An extra bit added to detect errors in transmission

 
### ■ *Parallel* parity checker

- Takes all inputs **simultaneously**
- Generates a parity bit using a combinational circuit
- Outputs 1 if okay and 0 otherwise



 
### ■ *Sequential* parity checker

- Takes a sequence of 0's and 1's as a single bit
- **Memorizes** all past inputs to generate a parity bit
- Outputs 1 if okay and 0 otherwise


 
## Example: Sequential Parity Checker


- States: only two states are sufficient
  - Used to remember whether the total number of 1 inputs received is even or odd
  - The initial state( $S_0$ ): an even number of 1 inputs have been received
  - The other state( $S_1$ ): an odd number of 1 inputs have been received
- State graph
  - If the circuit is in state  $S_0$  and  $X = 1$  is received, the circuit goes to state  $S_1$
  - ... ..



- Output for (even) parity checker
  - $Z = 0$  if the circuit is in state  $S_0$
  - $Z = 1$  if the circuit is in state  $S_1$
 
## Example: Sequential Parity Checker

- Wave form on when to take values as input
  - The value of  $X$  is read at the time of the active clock edge
  - The  $X$  input must be synchronized with the clock
  - The next should arrive before the next active clock edge
  - The clock is necessary to distinguish consecutive 0's or 1's on the input



## Example: Sequential Parity Checker

### ■ State and Transition Table (Symbolic version)

Present State	Next State		Present Output
	$X = 0$	$X = 1$	
$S_0$	$S_0$	$S_1$	0
$S_1$	$S_1$	$S_0$	1

### ■ State assignment

$$\begin{aligned} S_0 &\rightarrow 0 \\ S_1 &\rightarrow 1 \end{aligned}$$


### ■ State and Transition Table (Binary version)

$Q$	$Q^+$		$Z$	$T$	
	$X = 0$	$X = 1$		$X = 0$	$X = 1$
0	0	1	0	0	1
1	1	0	1	0	1

## Example: Sequential Parity Checker
 
### ■ T flip-flop implementation


- Flip-flop input equation  $T = X$
- Output equation  $Z = Q$



### ■ Initialization

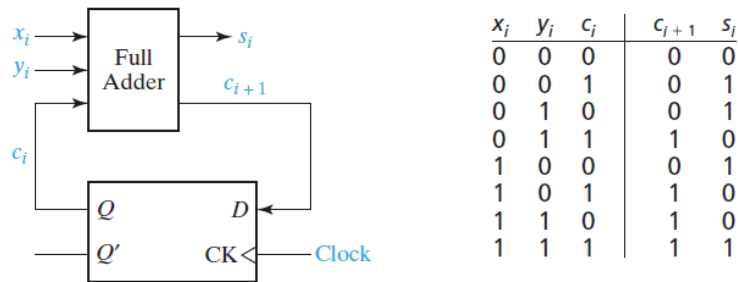
## Example: Serial Adder

- Adds two  $n$ -bit binary numbers
  - $X = x_{n-1} \dots x_1 x_0$ ,  $Y = x_{n-1} \dots x_1 x_0$
  - Two binary numbers are fed in serially, and the sum is read out serially
  - One pair of bits at a time
  - Carry should be saved for the next bit addition




## Example: Serial Adder

- Timing diagram
 
$$\begin{array}{r} 10011 \\ 00110 \\ \hline 11001 \end{array}$$


- State graph

 

## Procedure to Find the Output Sequence

---

1. Assume an initial state of the flip-flops (all flip-flops reset to 0 unless otherwise specified)
2. For the first input in the given sequence, determine the circuit output(s) and flip-flop inputs
3. Determine the new set of flip-flop states after the next active clock edge
4. Determine the output(s) that corresponds to the new states
5. Repeat 2, 3, and 4 for each input in the given sequence

## Procedure to Construct Transition Table

---

1. Determine the flip-flop input equations and output equations
2. Derive the next-state equation for each flip-flop using the characteristics equation
3. Plot a next-state map for each flip-flop
4. Combine these maps to form the transition table

## Moore vs. Mealy Machine

---

- *Moore machine*

- The output is a function of the present state only
- The state graph has the output associated with the state
- Example: sequential parity checker

## Moore vs. Mealy Machine


---

- *Mealy machine*

- The output is a function of both the present state and the input
- The state graph has the output associated with the arrow going between states
- Example: serial adder

## Analysis of a Moore Machine

### ■ Example circuit

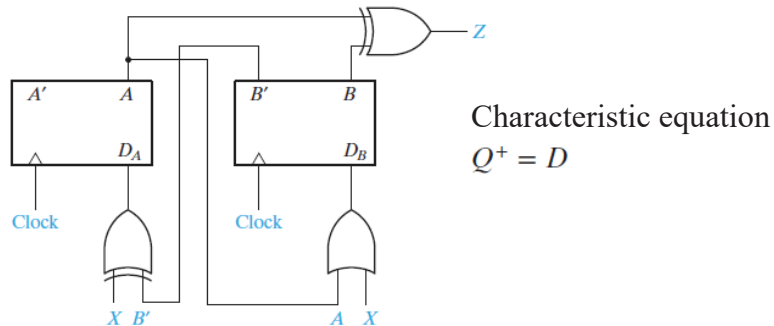

### ■ Flip-flop input equations, output equation

$$D_A = X \oplus B' \quad D_B = X + A \quad Z = A \oplus B$$

### ■ Next-state equations

$$A^+ = X \oplus B' \quad B^+ = X + A$$

## Analysis of a Moore Machine

### ■ Next-state maps

AB	X	
	0	1
00	1	0
01	0	1
11	0	1
10	1	0

$A^+$

AB	X	
	0	1
00	0	1
01	0	1
11	1	1
10	1	1

$B^+$


### ■ Transition table

AB	$A^+B^+$		Z
	X = 0	X = 1	
00	10	01	0
01	00	11	1
11	01	11	0
10	11	01	1

Present State	Next State		Present Output (Z)
	X = 0	X = 1	
$S_0$	$S_3$	$S_1$	0
$S_1$	$S_0$	$S_2$	1
$S_2$	$S_1$	$S_2$	0
$S_3$	$S_2$	$S_1$	1

# Analysis of a Moore Machine


## ■ State diagram

 

# Analysis of a Moore Machine
 
## ■ Timing diagram

- All state changes occur after the active edge
- The input is synchronized with the clock  $\Rightarrow$  the input assumes its next value after each active edge
- The output will only change when the state changes




$X =$	0	1	1	0	1	
$A =$	0	1	0	1	0	1
$B =$	0	0	1	1	1	1
$Z =$	(0)	1	1	0	1	0



## Analysis of a Mealy Machine

### ■ Example circuit

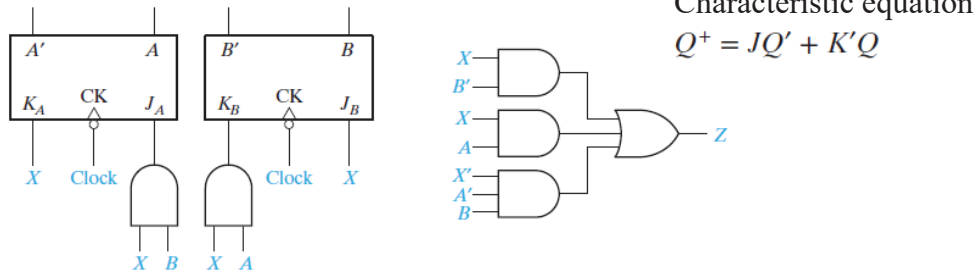

### ■ Flip-flop input equations

### ■ Next-state equations, output equation

$$A^+ = J_A A' + K_A' A = XBA' + X'A$$

$$B^+ = J_B B' + K_B' B = XB' + (AX)'B = XB' + X'B + A'B$$

$$Z = X'A'B + XB' + XA$$

## Analysis of a Mealy Machine

### ■ Next-state maps

		X	
		0	1
AB	00	0	0
	01	0	1
	11	1	0
	10	1	0

$A^+$

		X	
		0	1
AB	00	0	1
	01	1	1
	11	1	0
	10	0	1

$B^+$

		X	
		0	1
AB	00	0	1
	01	1	0
	11	0	1
	10	0	1

$Z$


### ■ Transition table

AB	$A^+B^+$		$Z$	
	X=0	1	X=0	1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1

Present State	Next State		Present Output	
	X=0	1	X=0	1
$S_0$	$S_0$	$S_1$	0	1
$S_1$	$S_1$	$S_2$	1	0
$S_2$	$S_2$	$S_0$	0	1
$S_3$	$S_3$	$S_1$	0	1

# Analysis of a Mealy Machine


## ■ State diagram

 

# Analysis of a Mealy Machine

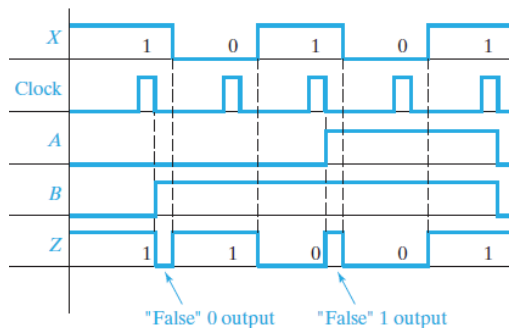
## ■ Timing diagram

- All state changes occur after the active edge
- The input changes right after the active edge
- The output will change when either the state or the input changes



$X = 1 \quad 0 \quad 1 \quad 0 \quad 1$   
 $A = 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0$   
 $B = 0 \quad 1 \quad 1 \quad 1 \quad 1 \quad 0$   
 $Z = 1(0) \quad 1 \quad 0(1) \quad 0 \quad 1$

## General Model For Mealy Circuit

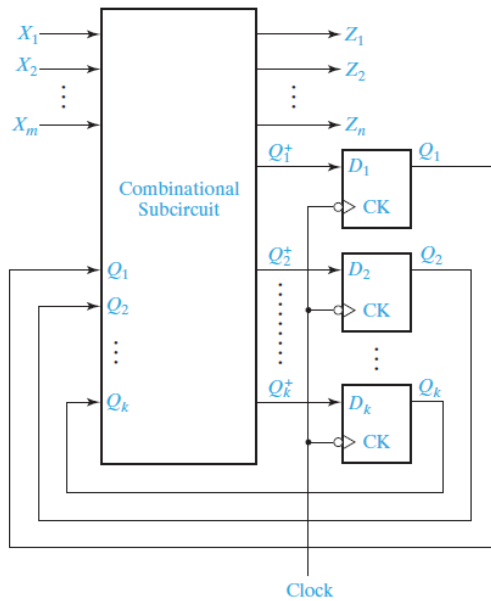

$n$  output functions

$$Z_1 = f_1(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

$$Z_2 = f_2(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

$\vdots$

$$Z_n = f_n(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

$k$  next-state functions


$$Q_1^+ = D_1 = g_1(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

$$Q_2^+ = D_2 = g_2(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

$\vdots$

$$Q_k^+ = D_k = g_k(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$

## General Model For Moore Circuit

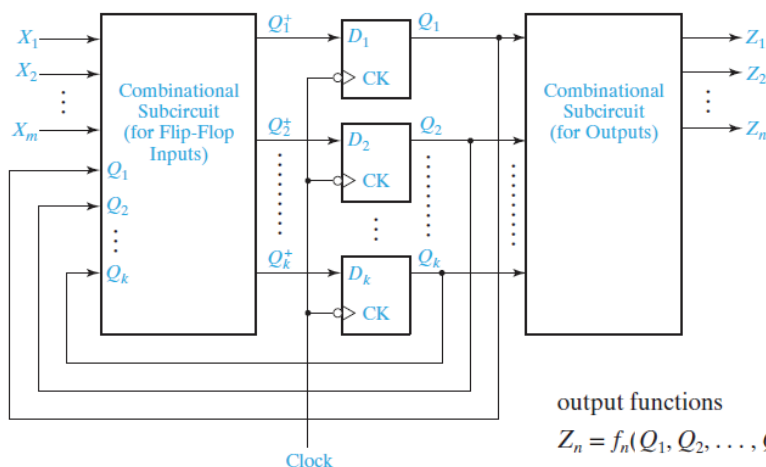

output functions

$$Z_n = f_n(Q_1, Q_2, \dots, Q_k)$$

next-state functions

$$Q_k^+ = D_k = g_k(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k)$$